

# **EE115C – Winter 2017**


## **Digital Electronic Circuits**

### **Lecture 17:**

## **Latches and Flip-Flops**



# Sequential Logic

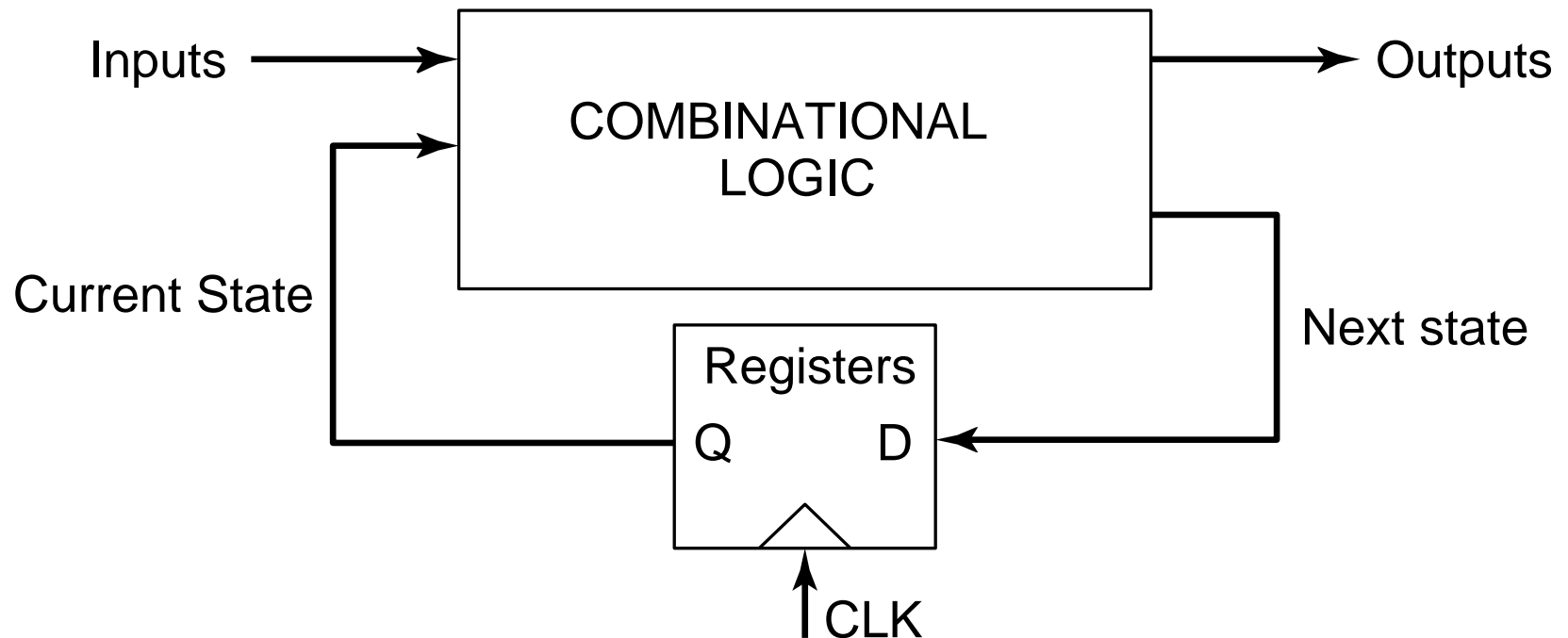

## ◆ 2 storage mechanisms



- Positive feedback
- Charge based

# Latch versus Flip-Flop

## ◆ Latch: level-sensitive

clock is low – hold mode



clock is high – transparent

  

## ◆ Flip-flop: edge-triggered

stores data when

clock rises

  

# Naming Convention


---

- ◆ **In this class:**
  - Latch is level sensitive
  - Flip-flop is edge-triggered
- ◆ **There are many different naming conventions**

 
# Latch-Based Design

- ◆ N latch is transparent when  $\Phi = 0$



- ◆ P latch is transparent when  $\Phi = 1$



# Positive Feedback: Bi-Stability

 


# Meta-Stability

  


**Gain should be larger than 1 in the transition region**
 
# Writing into a Static Latch

Use the clock as a decoupling signal,  
that distinguishes between the transparent and opaque states



**1** Converting into a MUX


 


**2** Forcing the state  
(can implement as NMOS-only)



# Cross-Coupled Pairs

## NOR-based set-reset

  



$S$	$R$	$Q$	$\bar{Q}$
0	0	$Q$	$\bar{Q}$
1	0	1	0
0	1	0	1
1	1	0	0

Forbidden State

## The “Overpowering” Approach

# Cross-Coupled NAND


## Cross-coupled NANDs

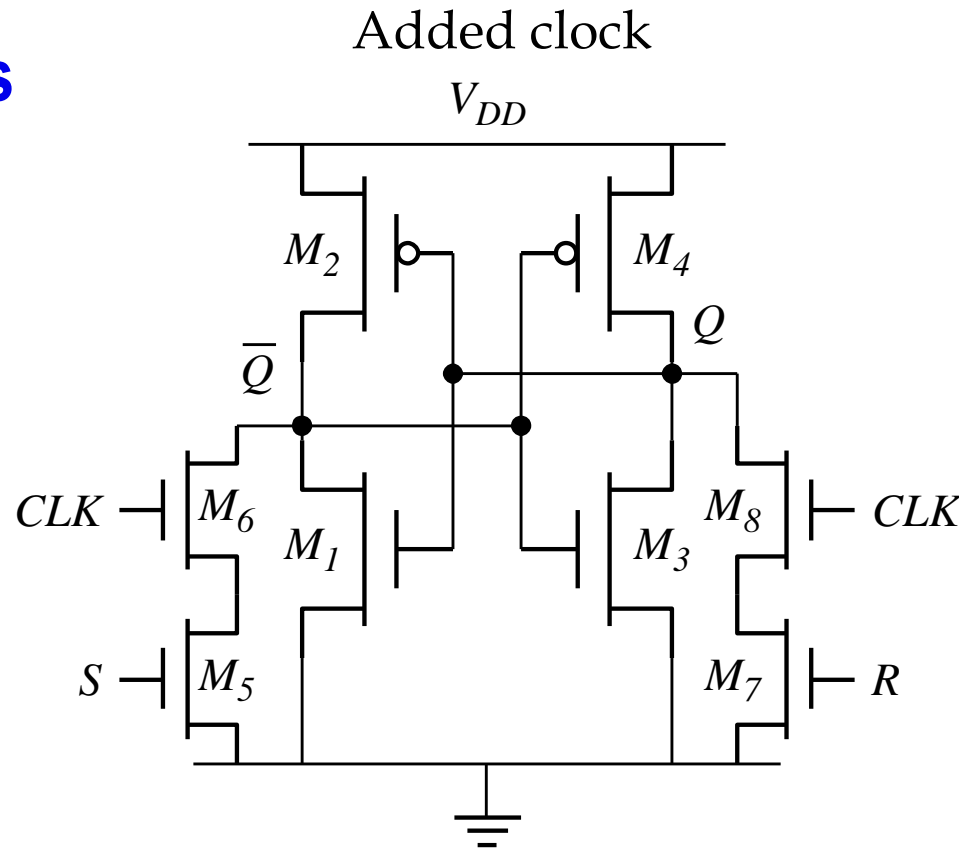 

This is not used in datapaths any more,  
but is a basic building memory cell


# Pseudo-Static Latch

---

 

 
# Mux-Based Latches

**Negative latch**  
(transparent when CLK= 0)




$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$

 **Positive latch**  
(transparent when CLK= 1)




$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$


# Mux-Based Latch

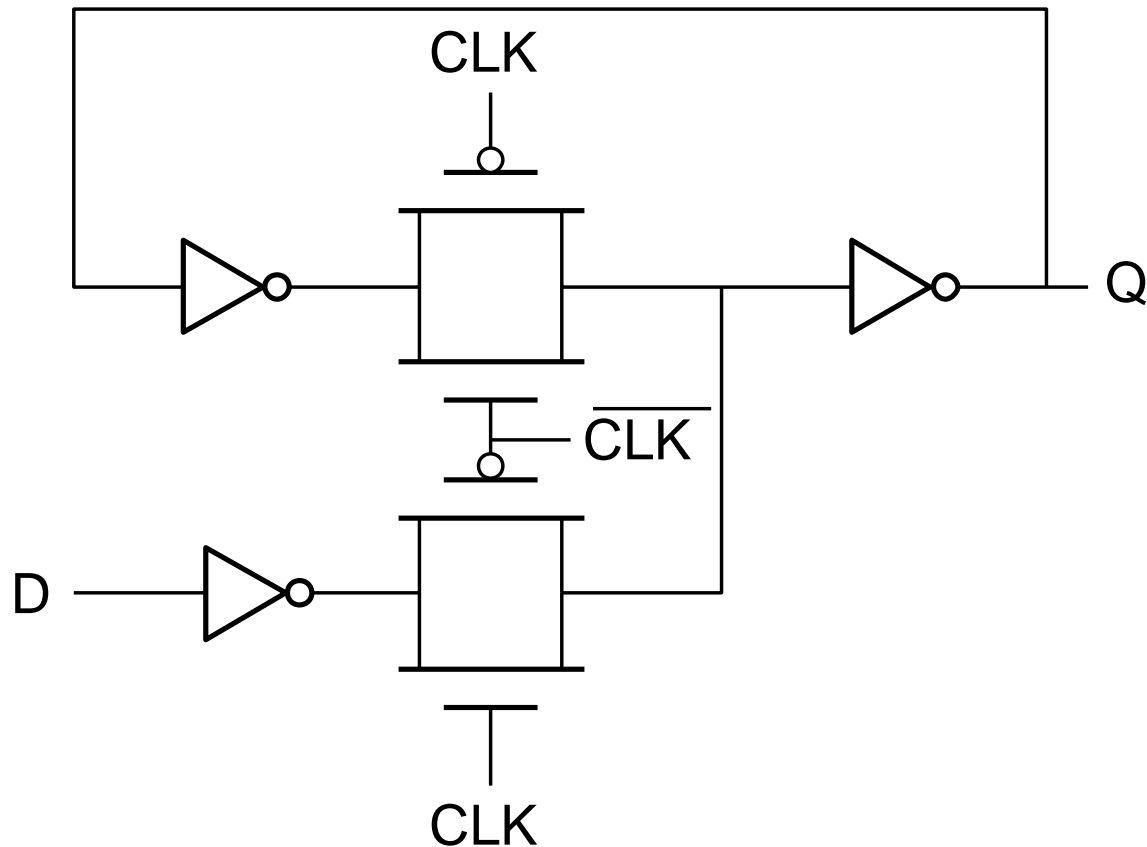

# Mux-Based Latch

 


NMOS only

 


Non-overlapping clocks

# Storage Mechanisms

## Static

 


## Dynamic

 


○ State node

# Pseudo-Static Latch

Dynamic

 

Pseudo-static

 




# Principal Ways to Build a Flip-Flop


---

Ways to design an edge-triggered sequential cell:


## Master-Slave Latches

 

## Pulse-Triggered Latch

 

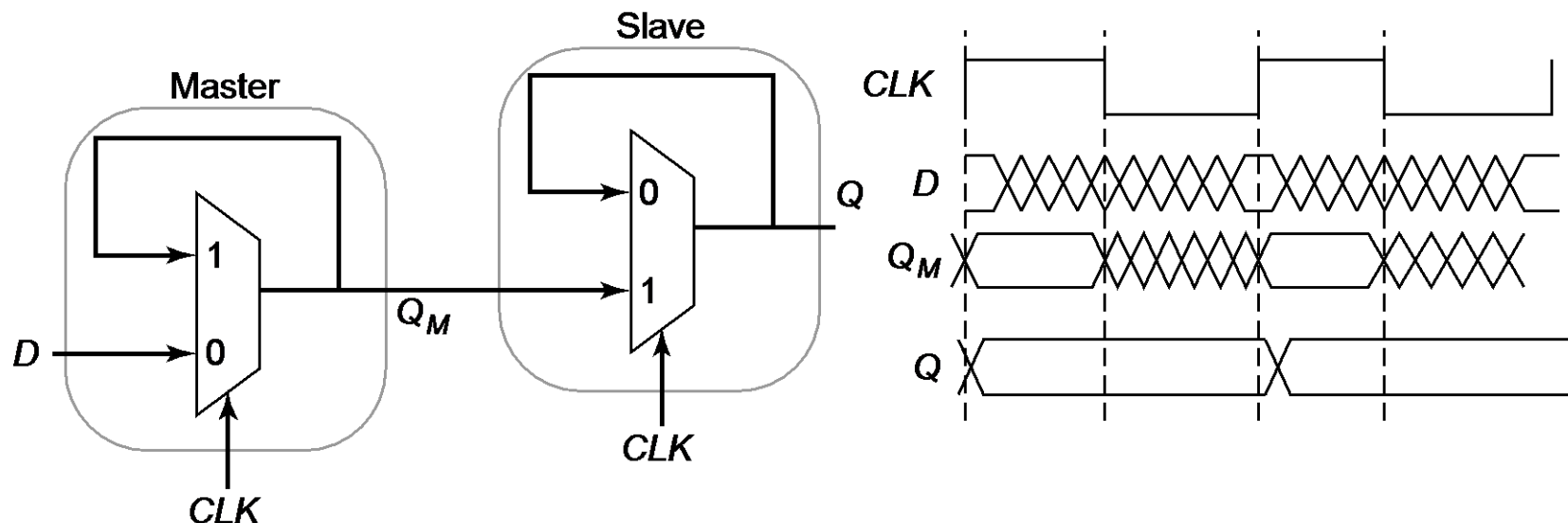
# Master-Slave (Edge-Triggered) Flip-Flop



Two opposite latches trigger on edge  
Also called master-slave latch pair


# Master-Slave Flip-Flop: Example

## Multiplexer-based latch pair

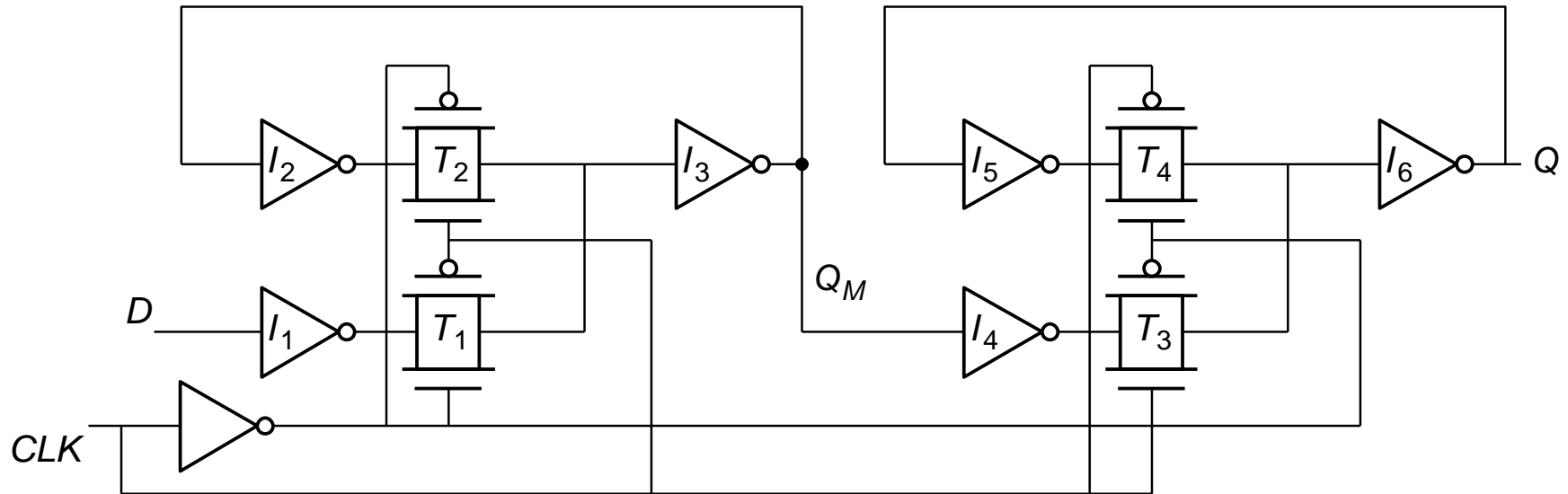

# Transmission-Gate Latches


## Simplest implementation

 

(a)

- only 4 transistors
- Dynamic when  $S=1$
- Susceptible to noise


## Basic static latch

 

(b)

- pull-up/pull-down keeper
- Conflict at node  $S$  whenever new data is written


## Complete implementation

 

(c)

- Feedback turned off when writing to the latch
- No conflict
- Larger clock load


# Transmission-Gate Flip-Flop

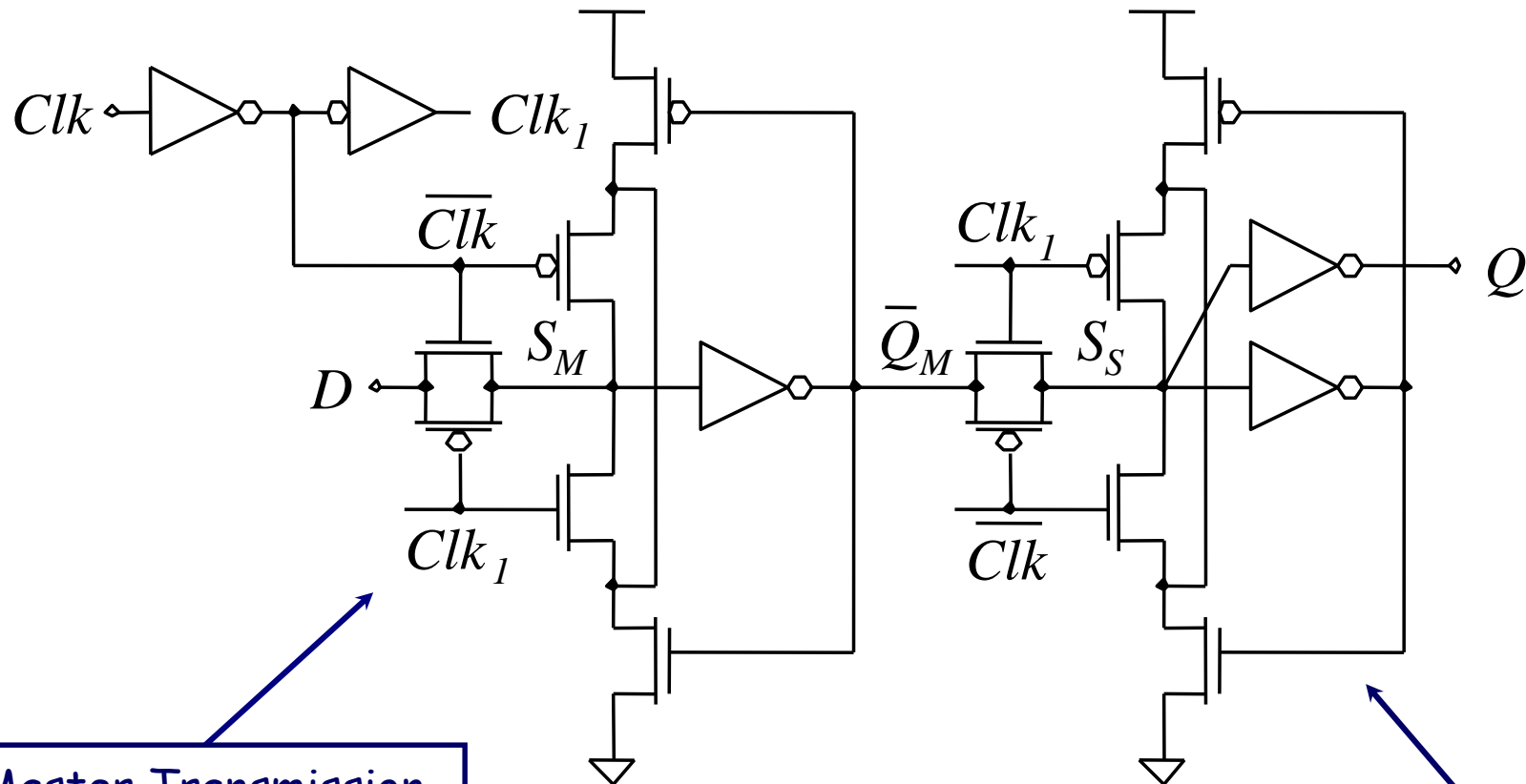

Master Transmission Gate Latch


Slave Transmission Gate Latch

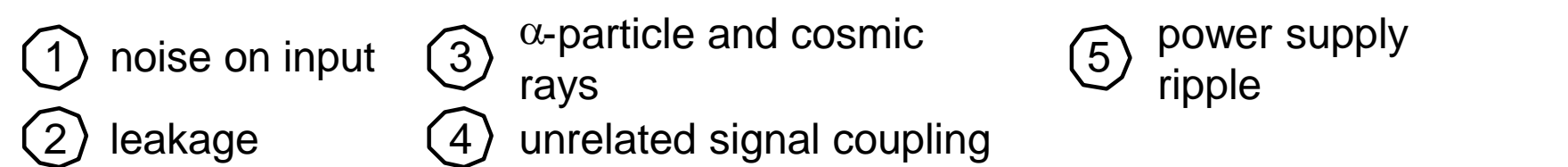*MSL with unprotected input  
(Gerosa et al. JSSC'94)*




### Sources of noise affecting the latch state node (Partovi in Chandrakasan et al. 2001)


# An Improved Version

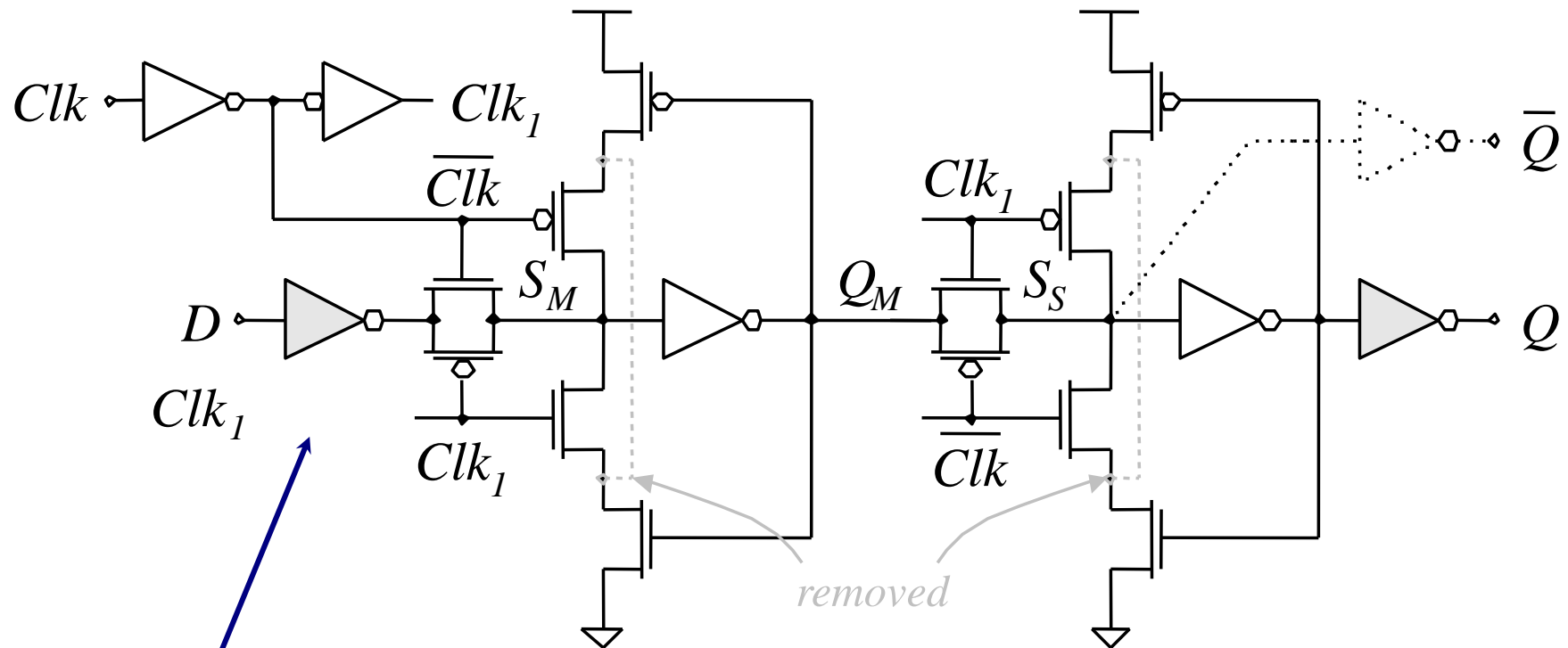

# Clocked CMOS (C<sup>2</sup>MOS) Latch

 

 
*Transmission gate latch with gate isolation (dynamic)*



*C<sup>2</sup>MOS latch (dynamic)*




# C<sup>2</sup>MOS Flip-Flop

 

Keepers can be added to staticize


# Static C<sup>2</sup>MOS Flip-Flop

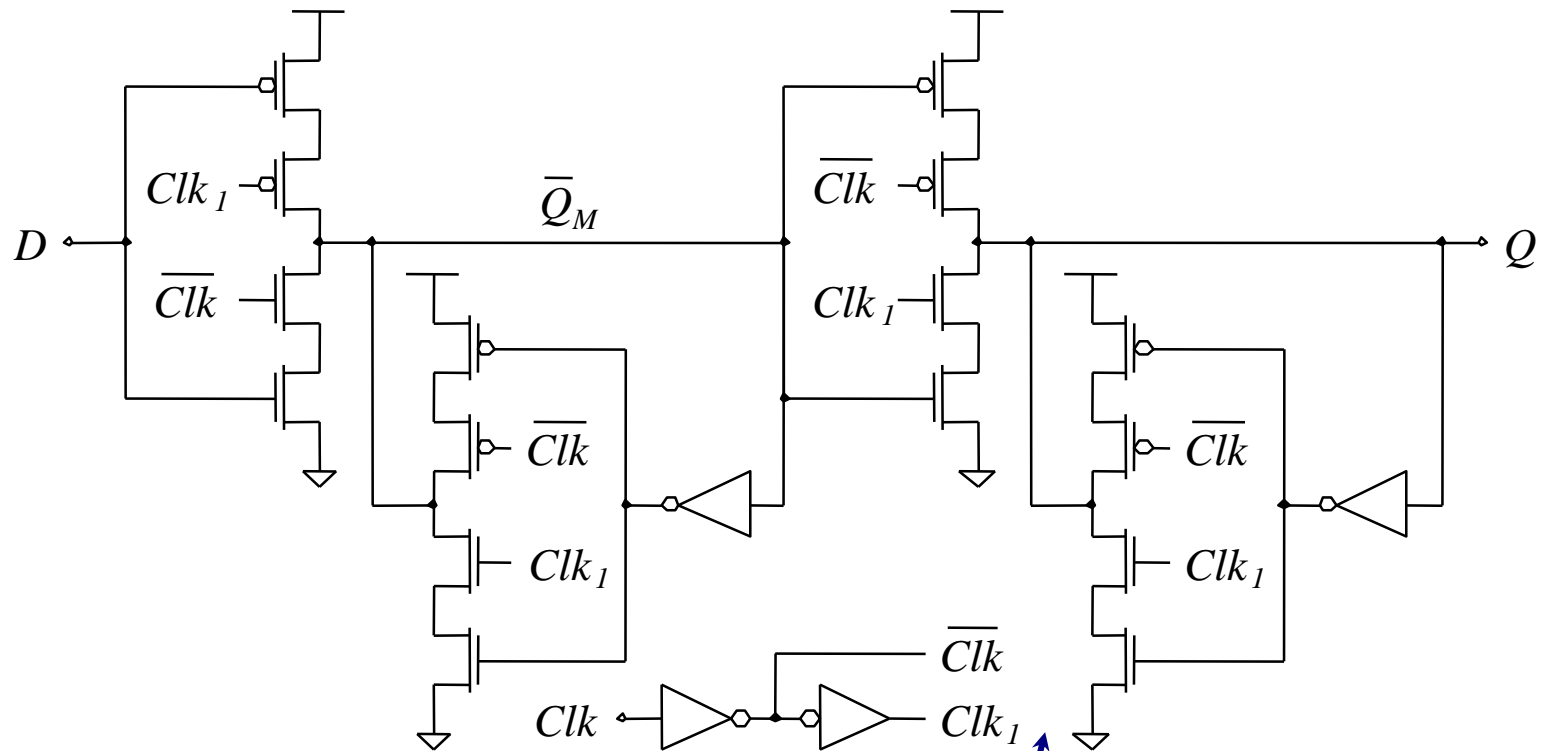


## State-keeping feedbacks outside the D-to-Q path

**(Suzuki et al. 1973)**

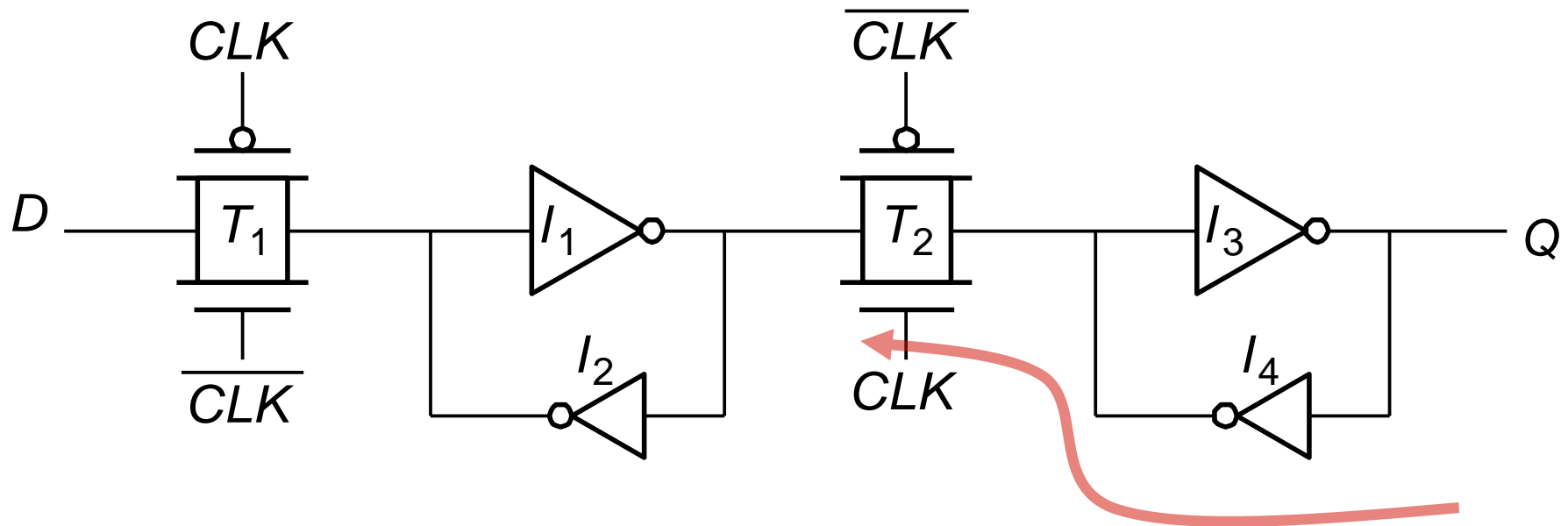
# Reduced Clock Load Master-Slave Flip-Flop



# Issue: Clock Overlap

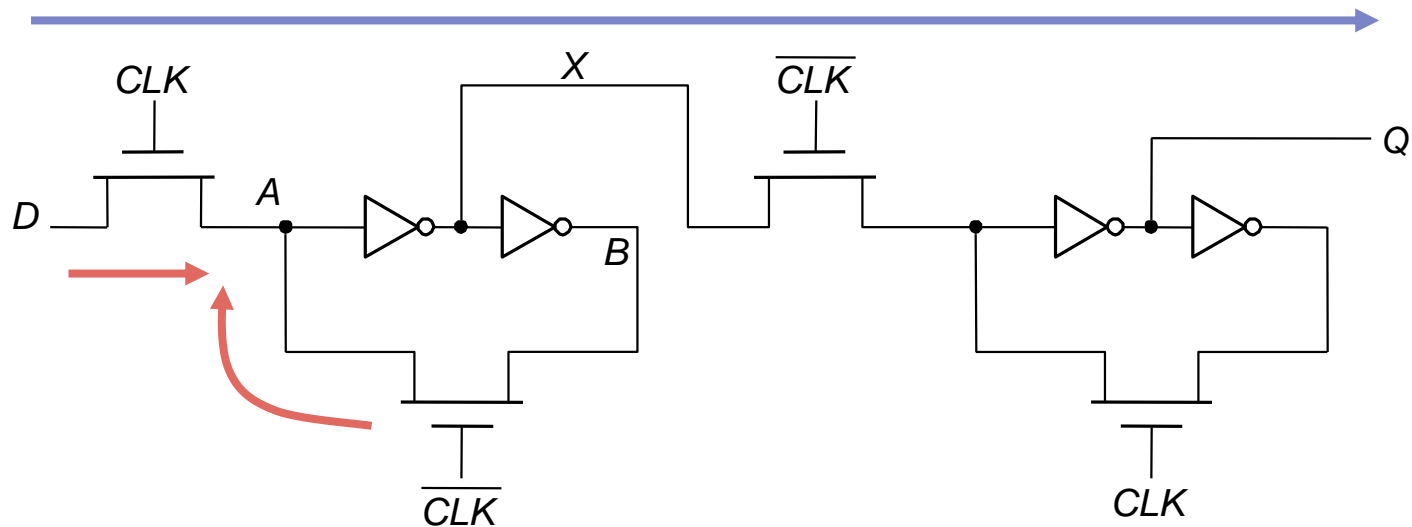


(a) Schematic diagram

 

(b) Overlapping clock pairs

 
# C<sup>2</sup>MOS Flip-Flop is Insensitive to Clock Overlap



Keepers can be added to staticize

 
# Pulsed latch: Intel's explicit pulsed latch

(Tschanz et al. 2001), Copyright © 2001 IEEE



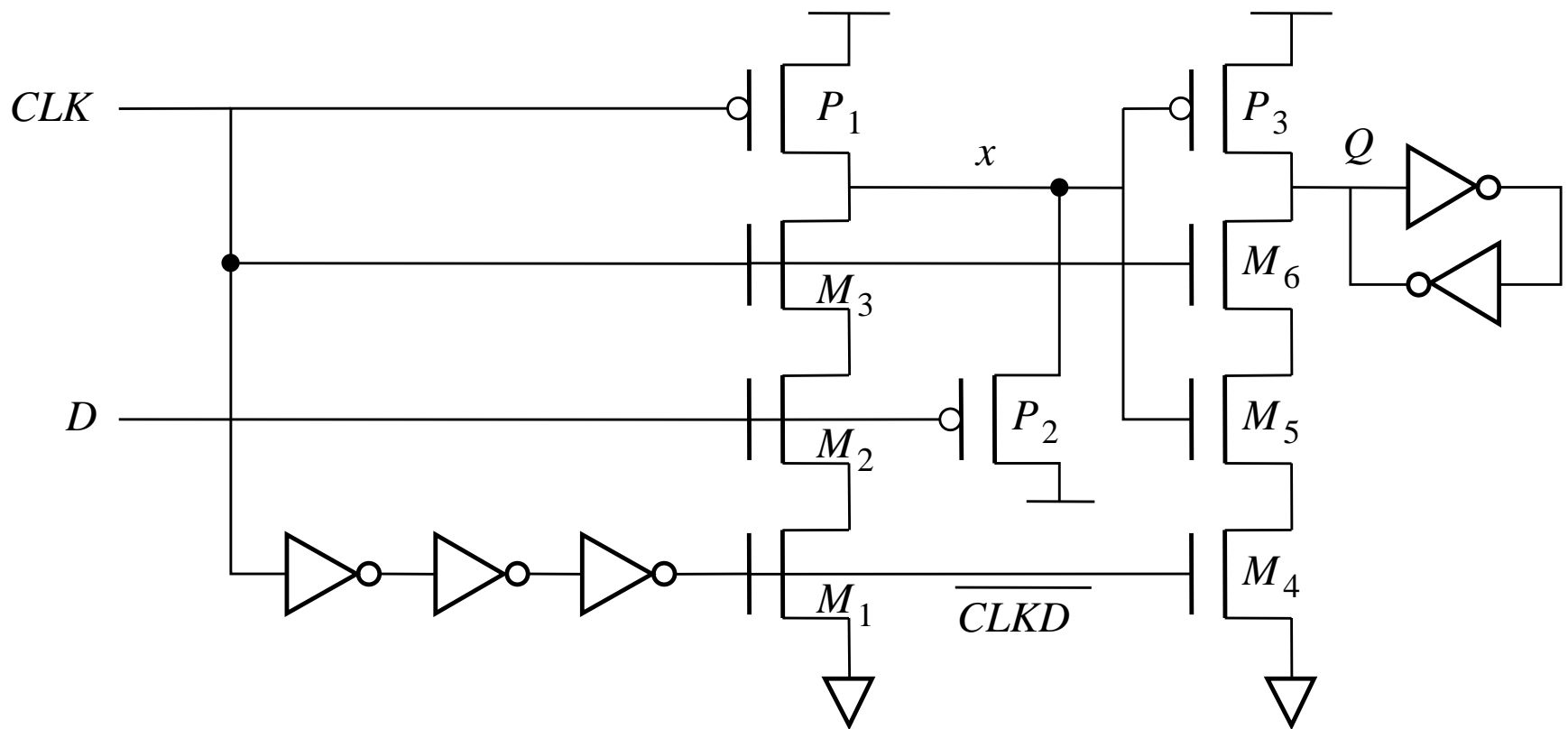
# AMD's Pulsed Latches

Hybrid Latch – Flip-flop (HLFF), AMD K-6 and K-7 :



# AMD's Hybrid Latch Flip-Flop (HLFF)

 

- Transparent to D only when Clk and  $\overline{\text{Clk1}}$  are both high
- Limited clock uncertainty absorption
- Small D $\rightarrow$ Q delay
- Small clock load

(Partovi et al. 1996), Copyright © 1996 IEEE